

Case Study 3: Boolean Circuit Equivalence

Step 1: Deriving Boolean Expressions

We start by analyzing the given Boolean circuits. Each gate is carefully traced to obtain the final expression.

Circuit (a):

- a) Input A passes through a NOT gate $\rightarrow A'$
- b) Input C passes through a NOT gate $\rightarrow C'$
- c) These are combined using AND $\rightarrow (A' \cdot C')$
- d) This output passes through a NOT gate $\rightarrow (A' \cdot C')'$
- e) By applying De Morgan's Law: $(A' \cdot C')' = A + C$
- f) Input B passes through a NOT gate $\rightarrow B'$
- g) A and B' are combined using AND $\rightarrow A \cdot B'$
- h) A, B' , and C are combined using AND $\rightarrow A \cdot B' \cdot C$
- i) OR operation between step (g) and step (h): $(A \cdot B') + (A \cdot B' \cdot C)$
- j) Simplify: $A \cdot B' + A \cdot C$

Final Expression for Circuit (a):

$$X = A \cdot B' + A \cdot C$$

Circuit (b):

- a) Input B passes through a NOT gate $\rightarrow B'$
- b) OR gate with C $\rightarrow B' + C$
- c) Input A AND with $(B' + C) \rightarrow A \cdot (B' + C)$
- d) Apply distributive law: $A \cdot B' + A \cdot C$

Final Expression for Circuit (b):

$$Y = A \cdot B' + A \cdot C$$

Step 2: Python Code Implementation

The Boolean circuits can be simulated using Python. The code accepts inputs A, B, and C, then prints outputs X (Circuit A) and Y (Circuit B):

```
# Case Study 3: Boolean Circuit Equivalence
# This program simulates two Boolean circuits and checks their outputs.

# Function for Circuit A
def circuit_a(A, B, C):
    a = not A      # Step a: NOT A
```

```

c = not C      # Step b: NOT C
temp1 = not (a and c) # Step c-d: (A'·C)
b_not = not B   # Step f: NOT B
e = A and b_not # Step g: A·B'
f = A and B and C # Step h: A·B·C
result = e or f   # Step i: (A·B') + (A·B·C)
return result

# Function for Circuit B
def circuit_b(A, B, C):
    b_not = not B   # Step a: NOT B
    temp1 = b_not or C # Step b: B' + C
    result = A and temp1 # Step c: A·(B' + C)
    return result

# Main program: User input
A = bool(int(input("Enter A (0 or 1): ")))
B = bool(int(input("Enter B (0 or 1): ")))
C = bool(int(input("Enter C (0 or 1): ")))

# Outputs
X = circuit_a(A, B, C)
Y = circuit_b(A, B, C)

# Print results
print("X (Circuit A) =", int(X))
print("Y (Circuit B) =", int(Y))

```

Step 3: Truth Tables and Testing

To confirm correctness, we generate truth tables for both circuits.

Truth Table for Circuit A (X):

The circuits can be represented in Python using Boolean logic operators.

A	B	C	X (Circuit A)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0

1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Truth Table for Circuit B (Y):

A	B	C	Y (Circuit B)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Testing with Console Outputs:

Testing is performed to confirm that both circuits consistently yield the same outputs. Each test case includes input, working explanation, expected output, and observed result.

Test Case 1: A=1, B=0, C=0

- **Input:** A=1, B=0, C=0
- **Working:** Substituting values into both circuits yields X=1 and Y=1.
- **Output:** X=1, Y=1
- **Result:** Pass

Console Output:

```
Enter A (0 or 1): 1
Enter B (0 or 1): 0
Enter C (0 or 1): 0
X (Circuit A) = 1
Y (Circuit B) = 1
```

Test Case 2: A=1, B=0, C=1

- **Input:** A=1, B=0, C=1
- **Working:** Both expressions evaluate to 1.
- **Output:** X=1, Y=1
- **Result:** Pass

Console Output:

```
Enter A (0 or 1): 1
Enter B (0 or 1): 0
Enter C (0 or 1): 1
X (Circuit A) = 1
Y (Circuit B) = 1
```

Test Case 3: A=1, B=1, C=0

- **Input:** A=1, B=1, C=0
- **Working:** Both circuits evaluate to 0.
- **Output:** X=0, Y=0
- **Result:** Pass

Console Output:

```
Enter A (0 or 1): 1
Enter B (0 or 1): 1
Enter C (0 or 1): 0
X (Circuit A) = 0
Y (Circuit B) = 0
```

Test Case 4: A=0, B=0, C=1

- **Input:** A=0, B=0, C=1
- **Working:** Both circuits evaluate to 0.
- **Output:** X=0, Y=0
- **Result:** Pass

Console Output:

```
Enter A (0 or 1): 0
Enter B (0 or 1): 0
Enter C (0 or 1): 1
X (Circuit A) = 0
Y (Circuit B) = 0
```

Step 4: Equivalence Verification

By comparing truth tables and test outputs, we observe:

- For **all possible input values** of A, B, and C, the outputs X and Y are identical.
- Both circuits simplify to the **same Boolean expression**: $A \cdot B' + A \cdot C$.
- This proves that **Circuit A and Circuit B are equivalent**.